Circuit check

ICT

Recognise that a complete circuit is needed for a device to work

- On the chart, explain why these bulbs will not light.

Circuit	The bulb will not light because ...
A	
B	
C	
D	
E	

- Re-draw circuits A and C so that the bulbs will light.
- Check them by making the circuits. Do the bulbs light?

Name _____ Worksheet 1a

Circuits and Conductors

Colour in yellow any bulb that will light up. Colour in black any bulb that will not light up.

© Windmill Press - Year Four Science - Photocopiable Resource