Changing circuits

Name.....

Look at each circuit diagram below. If you think the bulb or bulbs will light, put a tick in the box. If you do not think the bulb or bulbs will light, put a cross in the box.

1

2

3

4

5

6

key

⊗ = bulb |1 = battery Ⓜ = Motor O-O = closed switch O = open switch.